

# Pacemaker/defibrilator


Lkaa 2012

# Pacemaker



**Figure 13.6** Examples of early pacemakers (top row) and metal encapsulated devices (bottom row). The two units on the bottom right are modern pacemakers that are about the size and mass of a pocket watch. (Photograph courtesy of Medtronic Corp.).

# Pacemaker

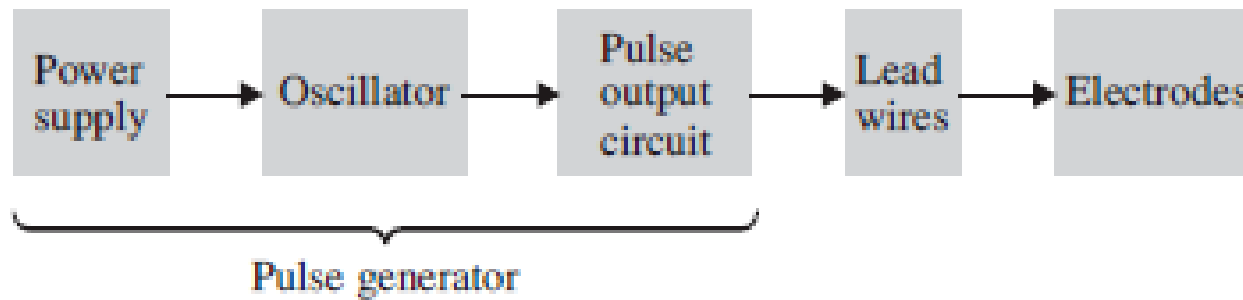


**Figure 13.1** Block diagram of an asynchronous cardiac pacemaker

# Pacemaker


- Litium batterier
- 5,0 til 5,5V
- 8 til 10 mA
- 1,0 til 1,2 ms
- 70 til 90 slag/min

# Synkron pacemaker

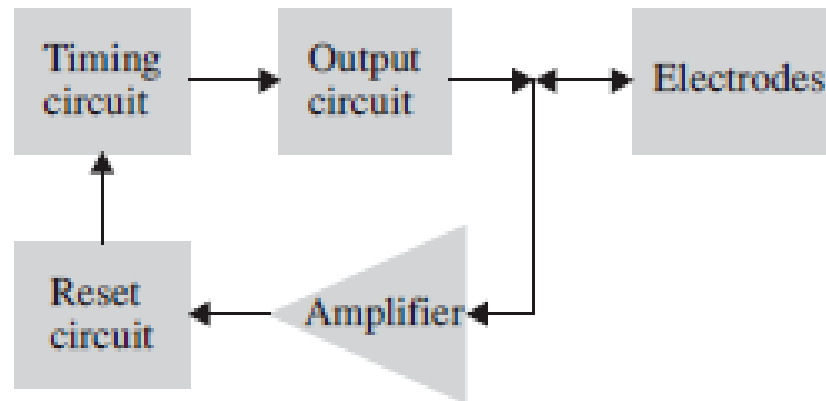


**Figure 13.3** A demand-type synchronous pacemaker Electrodes serve as a means of both applying the stimulus pulse and detecting the electric signal from spontaneously occurring ventricular contractions that are used to inhibit the pacemaker's timing circuit.

# Atrial synkron

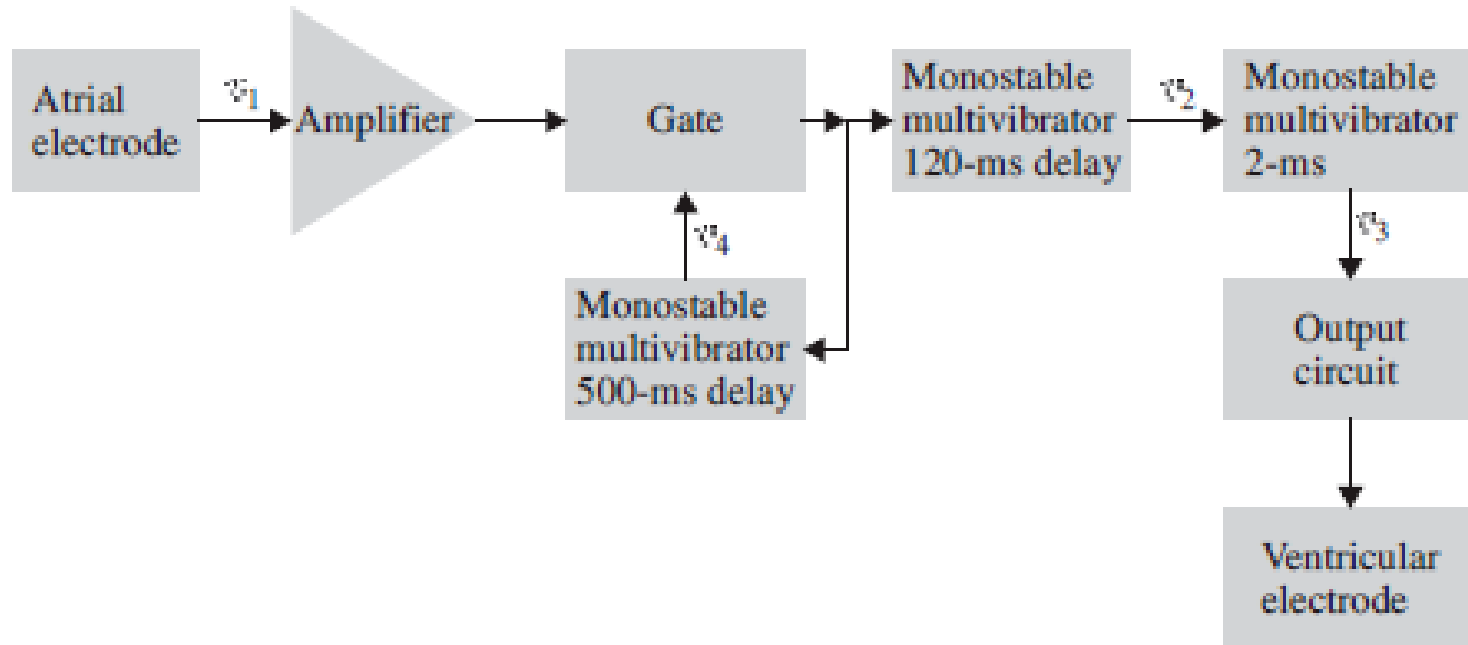


**Figure 13.4** An atrial-synchronous cardiac pacemaker, which detects electric signals corresponding to the contraction of the atria and uses appropriate delays to activate a stimulus pulse to the ventricles.

# Hjertestarter

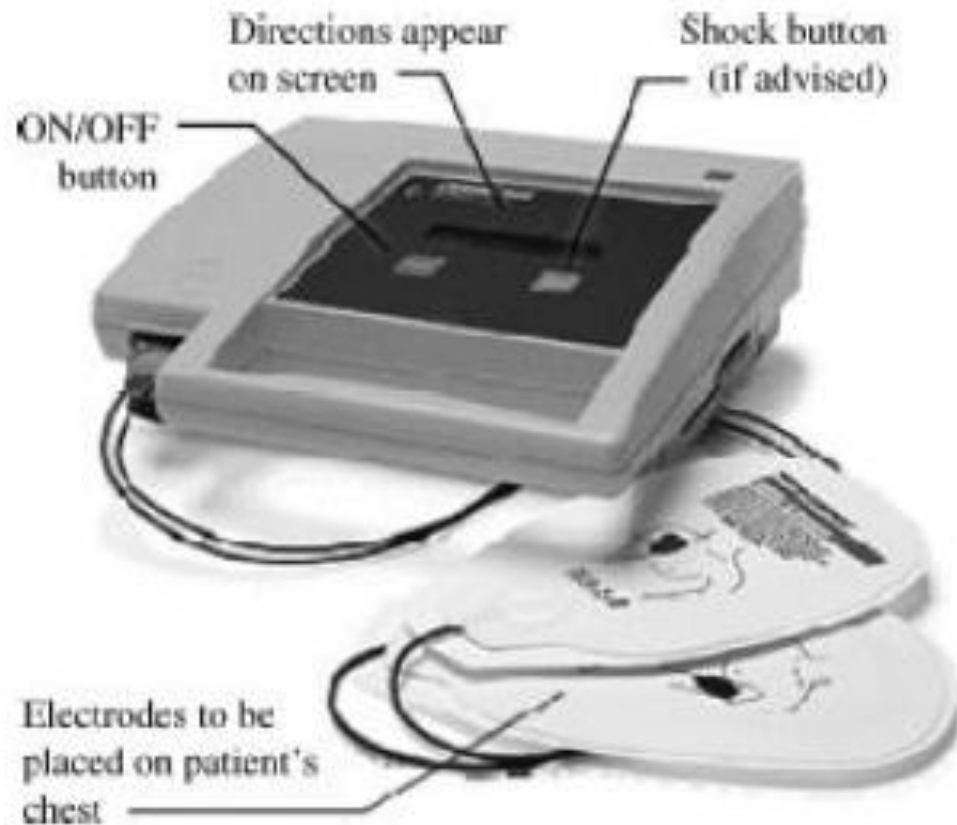

# Defibrillator

$$E = \frac{Cv^2}{2} \quad (13.4)$$

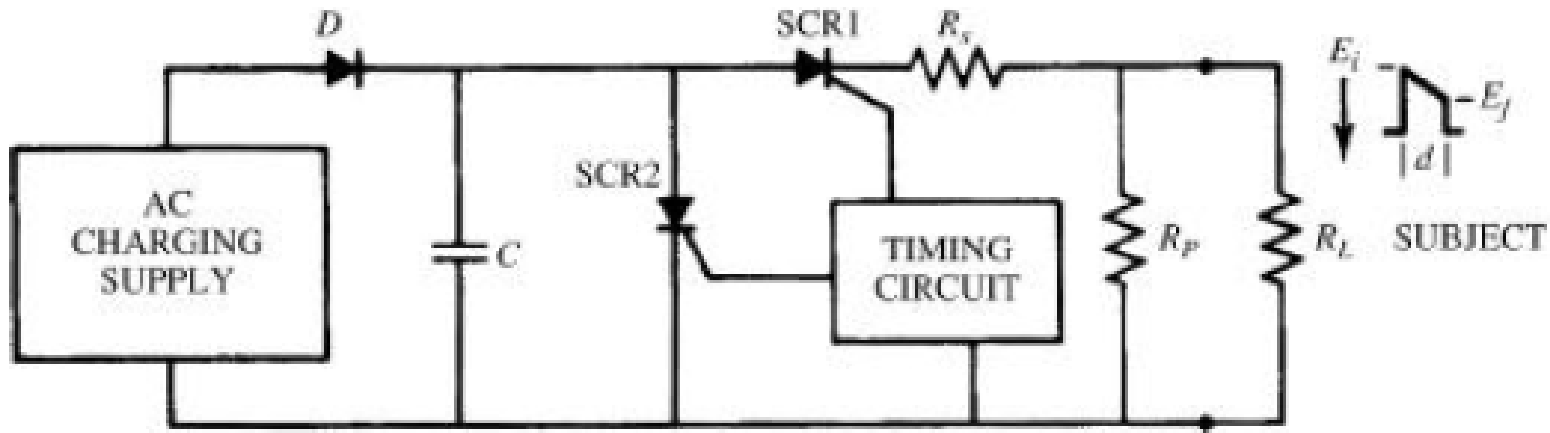

**Figure 13.10** The square and trapezoidal waveform defibrillator may have a battery that drives the ac charging supply. Diode  $D$  rectifies the ac to charge capacitor  $C$ . Series  $SCR1$  is turned on to deliver current to subject  $R_L$ . The timing circuit calculates the charge delivered, then after duration  $d$ , shunt  $SCR2$  short circuits the charge. [From Geddes (1984).].



$$E = \frac{v^2}{R_L} \int_0^t e^{-\frac{2t}{R_L C}} dt \quad (\text{E13.7})$$

90% of this energy will be dissipated by

$$e^{-\frac{2t}{R_L C}} = 0.1 \quad (\text{E13.8})$$

or

$$t = R_L C \frac{\ln(0.1)}{2} \quad (\text{E13.9})$$


Because  $t$  is required to be 8 ms

$$C = -\frac{2t}{R_L [\ln(0.1)]} = \frac{-2 \times 8 \times 10^{-3} \text{ s}}{100 \Omega \times [-2.3]} = 69.6 \mu\text{F} \quad (\text{E13.10})$$

(b) We can now determine the voltage to which the capacitor should be charged from (E13.6)

$$v = \sqrt{\frac{2E_t}{C}} = \sqrt{\frac{2 \times 300 \text{ J}}{69.6 \times 10^{-6} \text{ F}}} = 2,940 \text{ V} \quad (\text{E13.11})$$

# Cardioverter

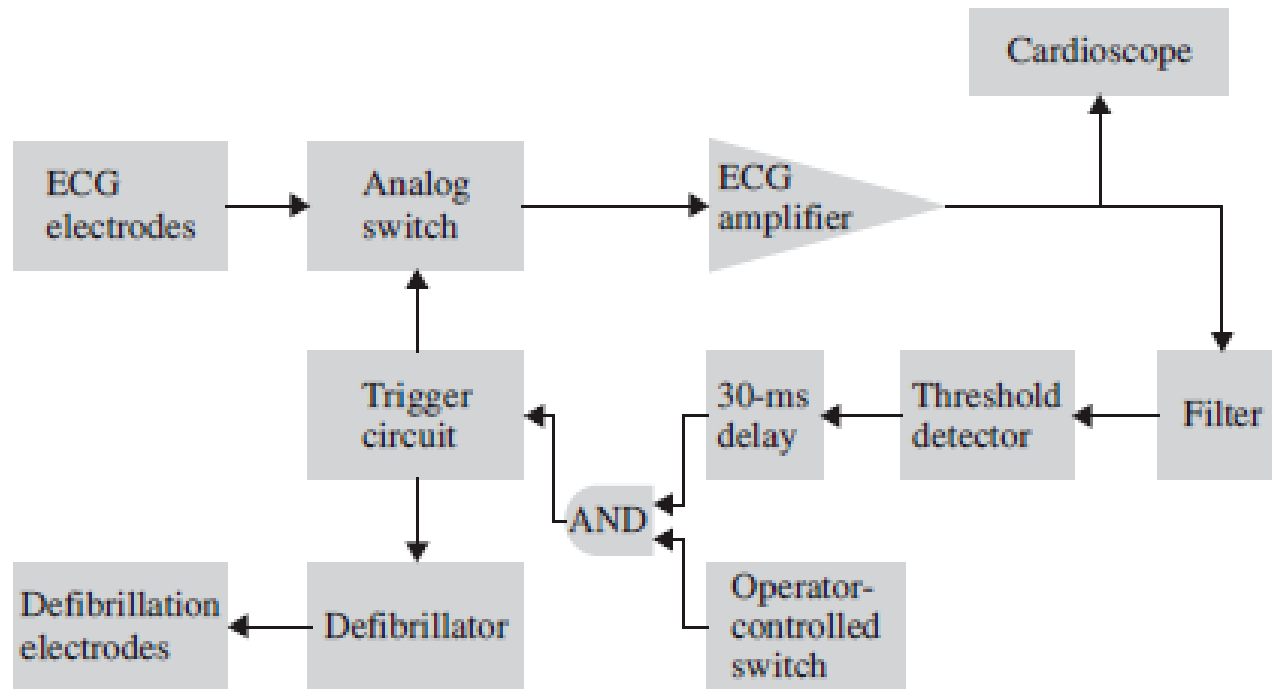

**Figure 13.12** In a cardioverter, the defibrillation pulse must be synchronized with the R wave of the ECG so that it is applied to a patient shortly after the occurrence of the R wave.